FPGA Assignment

Kanike Bhavani bhavani7013313986@gmail.com IITH Future Wireless Communication (FWC)

FWC22017

ASSIGN

Problem

Draw the logic circuit of the following Boolean Expression using only NAND Gates : X.Y + Y.Z;

Components

Components	Values	Quantity
Vaman		1
JumperWires	M-F	5
Breadboard		1
USB-C cable		1
LED		1

1 Setup

- 1. Connect the Vaman to the Laptop through USB.
- 2. There is a button and an LED to the left of the USB port on the Vaman. There is another button to the right of the LED.
- 3. Press the right button first and immediately press the left button. The LED will be blinking green. The Vaman is now in bootloader mode.

1.1 Steps for implementation

1. Login to termux-ubuntu on the android device and execute the following commands:

Make sure that the required installation and tool builds of pygmy-sdk had done prior executing below commands

proot—distro login debian
cd /data/data/com.termux/files/home/
mkdir fpga
svn co https://github.com/gowripriya—2002/trunk/
fpga/codes
cd codes
ql_symbiflow —compile —src /data/data/com.termux

ql_symbiflow —compile —src /data/data/com.termux /files/home/fpga/codes —d ql—eos—s3 —P PU64 —v helloworldfpga.v —t helloworldfpga —p quickfeather.pcf —dump binary

This will generate **helloworldfpga.bin** file in codes directory transfer this bin file to laptop by executing the following command

scp /data/data/com.termux/files/home/fpga/codes/ helloworldfpga.bin username_of_pc@IP_address:/ home/username Make sure that the appropriate username, IP address of the Laptop is given in the above command.

2. Now execute the following commands on the Laptop terminal

Make sure that required installation of programmer application had done prior executing below command

python3 /home/username/TinyFPGA—Programmer— Application/tinyfpga—programmer—gui.py — port /dev/ttyACM0 ——appfpga /home/ username/helloworldfpga.bin ——mode fpga

 After finishing the process of flashing with the programmer application press the button to the right of the USB port to reset. Vaman is now flashed with our source code

Implementation

$$F = XY + YZ \tag{1}$$

Implementing above boolean function using NAND gates only

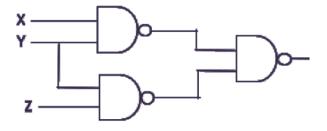


Figure 1: circuit

Truth Table

Х	Y	Z	F
0	0	0	0
0	0	1	0
0	1	1	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

Truth Table

The code below realizes the Boolean logic for F using 5V,GND of Vaman Board using Verilog Language

https://github.com/bhavani360/FWC_assignments/fpga/codes/helloworldfpga.v